



Gisselquist  
Technology, LLC

## 2. Registers

Daniel E. Gisselquist, Ph.D.





# Lesson Overview



## ▷ Lesson Overview

Registers  
Memoryless Regs  
Flip Flops  
Blocking  
All in Parallel  
Feedback  
Blinky  
Broken Blinky  
Verilator  
Verilator  
Verilator  
Parameters  
Sim Result  
Trace Generation  
GTKWave  
Strobe  
Toggled  
PPS  
Stretch  
Too Slow  
Dimmer  
Exercise #1  
Exercise #2

- What is a register (**reg**)?
- How do things change with time?
- Discover the system clock

## Objectives

- Something



# Registers



Lesson Overview

▷ Registers

Memoryless Regs

Flip Flops

Blocking

All in Parallel

Feedback

Blinky

Broken Blinky

Verilator

Verilator

Verilator

Parameters

Sim Result

Trace Generation

GTKWave

Strobe

Toggled

PPS

Stretch

Too Slow

Dimmer


Exercise #1

Exercise #2

- Wires have no memory
  - Only registers can hold state
- Well, that and memories, but we haven't gotten to those yet



# Memoryless Regs

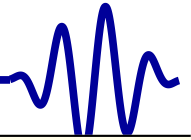

- Lesson Overview
- Registers
  - Memoryless
    - ▷ Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
reg      [7:0]  A;


always  @(*)
        A = 9'h87;

assign  o_led = A ^ i_sw;
```

- Registers can be assigned in always blocks.
- Always blocks may consist of one statement, or
- Many statements between a **begin** and **end** pair



# Flip Flops

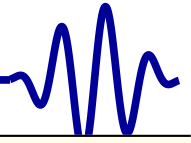

- Lesson Overview
- Registers
- Memoryless Regs
- ▷ Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
reg      [9:0]  A;

always  @(posedge i_clk)
    A <= A + 1'b1;
```

- Any registers set within an **always** @(posedge i\_clk) block will transitions to their new values on the next clock edge only
  - *Only put a bonafide clock edge should be used*
- Note that we are using <= for assignment
  - This is a *non-blocking* assignment
  - Most, if not all, clocked register should be set with <=



# Blocking



- This is a non-blocking assignment

```
always @(posedge i_clk)
    A <= A + 1'b1;
```

- Blocking assignment

```
always @(posedge i_clk)
    A = A + 1'b1;
```

- A blocking assignment's value may be referenced again before the clock edge
  - Creates the appearance of time passing within the block
  - *It may also cause simulation-hardware mismatch*
  - *Use with caution*
- In this case, both generate the same logic



# All in Parallel



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- ▷ All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

- A design may contain multiple always blocks
- The hardware will execute all at once
- The simulator will execute one at a time

Rules: When using the simulator, ...

- Make sure your design can be synthesized
- Make sure it fits within your device
- Make sure it maintains an appropriate clock rate



# Feedback



Lesson Overview  
Registers  
Memoryless Regs  
Flip Flops  
Blocking  
All in Parallel  
▷ Feedback  
Blinky  
Broken Blinky  
Verilator  
Verilator  
Verilator  
Parameters  
Sim Result  
Trace Generation  
GTKWave  
Strobe  
Toggled  
PPS  
Stretch  
Too Slow  
Dimmer  
Exercise #1  
Exercise #2

- Wires in a loop created circular logic
- Registers in a loop creates feedback





# Blinky



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- ▷ Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

Let's make an LED blink!

```
module blinky(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1'b1;  
  
    assign   o_led = counter[26];  
endmodule
```

Feel free to synthesize and try this

- The LED should blink at a steady rate



# Broken Blinky



Don't do this: Here's a common beginner mistake

```
reg        counter;  
always @(posedge i_clk)  
    counter <= counter + 1'b1;  
assign    o_led = counter;
```

- Notice that counter is only 1-bit
- This will blink at half the i\_clk frequency
- Result is too fast to see the changes
- Need to slow it down

Lesson Overview  
Registers  
Memoryless Regs  
Flip Flops  
Blocking  
All in Parallel  
Feedback  
Blinky  
▷ Broken Blinky  
Verilator  
Verilator  
Verilator  
Parameters  
Sim Result  
Trace Generation  
GTKWave  
Strobe  
Toggled  
PPS  
Stretch  
Too Slow  
Dimmer  
Exercise #1  
Exercise #2



# Verilator



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- ▷ Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

Simulating our design now requires a clock:

```
void      tick(Vblinky *tb) {  
    // The following eval() looks  
    // redundant ... many of hours  
    // of debugging reveal its not  
    tb->eval();  
    tb->i_clk = 1;  
    tb->eval();  
    tb->i_clk = 0;  
    tb->eval();  
}
```

- We'll need to toggle the clock input for anything to happen
- This operation is so common, it deserves its own function, **tick()**



# Verilator



We can now simplify our main loop a touch

```
int main(int argc, char **argv) {  
    int last_led;  
    // .... Setup  
  
    last_led = tb->o_led;  
    for(int k=0; k<(1<<20); k++) {  
        // Toggle the clock  
        tick(tb);  
  
        // Now let's print the LEDs value  
        // anytime it changes  
        if (last_led != tb->o_led) {  
            printf("k_=%7d, ", k);  
            printf("led_=%d\n", tb->o_led);  
        } last_led = tb->o_led;  
    }  
}
```



# Verilator



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
  - ▷ Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

Can we simulate this? Not easily


- Counting to  $2^{27}$  may take seconds in hardware, but ...
- It's extreme slow in simulation. Let's slow blinky down in the Sim.
- We can do this by adjusting the width of the counter

We'll use a parameter to do this

```
parameter          W=27;
reg                [W-1:0] counter;
// .....
assign o_led = counter[W-1];
```



# Parameters

 

- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- ▷ Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

Parameters are very powerful! They allow us to


- Reconfigure a design, after it's been written
- Examples:
  - ZipCPU cache sizes can be adjusted by parameters
  - Internal memory sizes, implement the divide instruction or not, specify the type of multiply
  - Default serial port speed, number of GPIO pins supported by a GPIO controller, and more

Verilator argument `-GW=12` sets the `W` parameter to 12

```
% verilator -Wall -GW=12 -cc blinky.v
```



# Sim Result

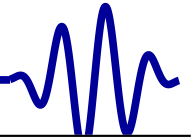


- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- ▷ Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
% ./blinky
k =      2047 , led = 1
k =      4095 , led = 0
k =      6143 , led = 1
k =      8191 , led = 0
k =     10239 , led = 1
k =     12287 , led = 0
k =     14335 , led = 1
k =     16383 , led = 0
k =     18431 , led = 1
k =     20479 , led = 0
# .... (Lines skipped for brevity)
%
```



# Trace Generation

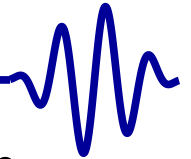

- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
  - Trace
- ▷ Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

This is easy. For more complex designs, we'll need a trace

- That means writing to a trace file on every clock

## Steps

1. Add the `--trace` option to Verilator
2. Create a trace from your `.cpp` file

```
#include "verilated_vcd_c.h"
// ...
int main(int argc, char **argv) {
    // ...
    unsigned tickcount = 0;
    // ...
}
```





# Trace Generation



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
  - Trace
- ▷ Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

Create the trace file within C++

```
// ...
int main(int argc, char **argv) {
    // ...
    // Generate a trace
    Verilated::traceEverOn(true);
    VerilatedVcdC* tfp = new VerilatedVcdC;
    tb->trace(tfp, 00);
    tfp->open("blinkytrace.vcd");

    // ...
    for(int k=0; k<(1<<20); k++) {
        tick(++tickcount, tb, tfp);
        // ...
    }
}
```



# Trace Generation



## 3. Write trace data on every clock

```
void    tick(int tickcount, Vblinky *tb,
            VerilatedVcdC* tfp) {
    tb->eval();
    if (tfp)
        tfp->dump(tickcount * 10 - 2);
    tb->i_clk = 1;
    tb->eval();
    if (tfp)
        tfp->dump(tickcount * 10);
    tb->i_clk = 0;
    tb->eval();
    if (tfp) {
        tfp->dump(tickcount * 10 + 5);
        tfp->flush();
    }
}
```



# Trace Generation



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
  - Trace
- ▷ Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

- Now, running blinky will generate a trace


```
% ./blinky  
# . . .
```

- You can view it with GTKwave


```
% gtkwave blinkytrace.vcd
```



# GTKWave

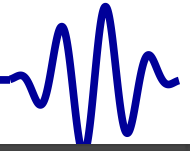

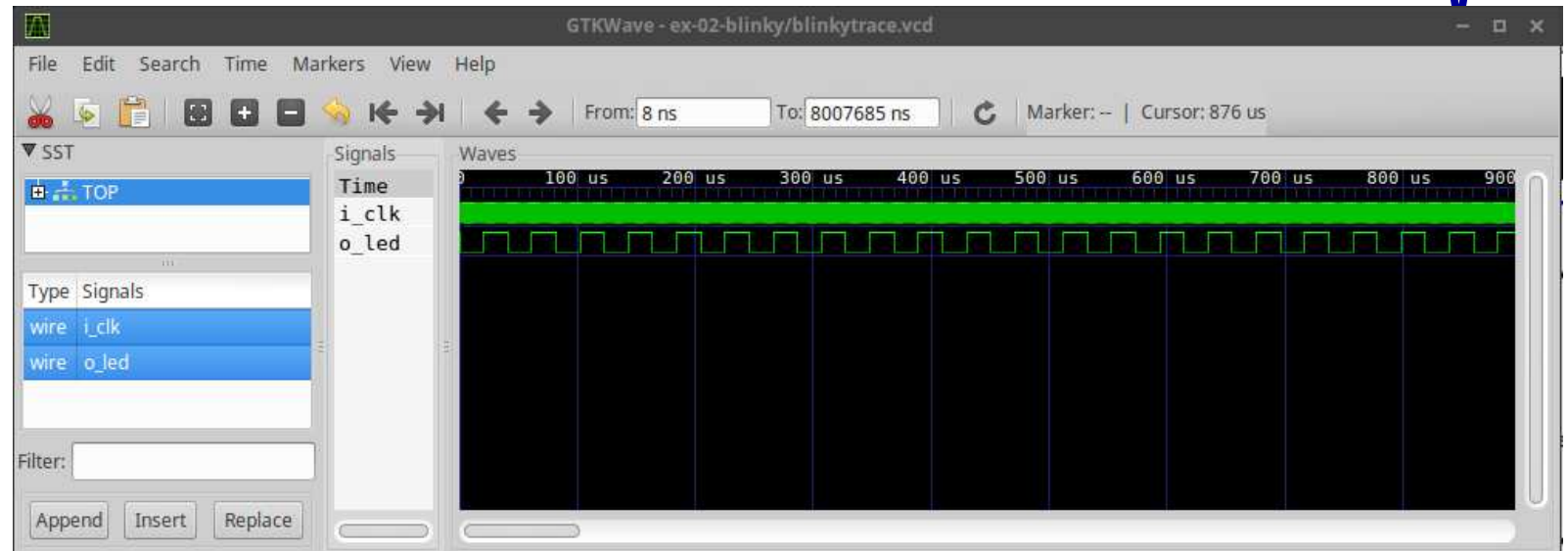Lesson Overview  
Registers  
Memoryless Regs  
Flip Flops  
Blocking  
All in Parallel  
Feedback  
Blinky  
Broken Blinky  
Verilator  
Verilator  
Verilator  
Parameters  
Sim Result  
Trace Generation  
▷ GTKWave  
Strobe  
Toggled  
PPS  
Stretch  
Too Slow  
Dimmer  
Exercise #1  
Exercise #2




This is how debugging is done

- The simulator trace shows you every registers value
- ... at every clock tick
- You can zoom in to find any bugs



# Strobe

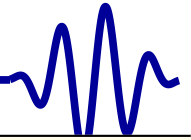


- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
  - ▷ Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
module strobe(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1'b1;  
  
    assign   o_led = &counter[26:24];  
endmodule
```



# Toggled

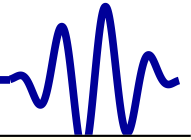


- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- ▷ Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
module blinky(i_clk, i_sw, o_led);  
    input    wire    i_clk, i_sw;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
    if (i_sw)  
        counter <= counter + 1'b1;  
  
    assign   o_led = counter[26];  
endmodule
```




# PPS

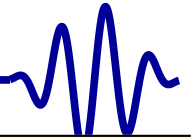

- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- ▷ PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
module pps(i_clk, o_led);  
    parameter CLOCK_RATE_HZ = 100_000_000;  
    parameter [31:0] INCREMENT  
                = (1<<30)/(CLOCK_RATE_HZ / 4);  
  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [31:0]   counter;  
  
    always @(posedge i_clk)  
            counter <= counter + INCREMENT;  
  
    assign   o_led = counter[31];  
endmodule
```

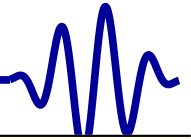- After CLOCK\_RATE\_HZ clock edges, the counter will roll over



```
parameter CLOCK_RATE_HZ = 100_000_000;  
parameter [31:0] INCREMENT  
               = (1<<30)/(CLOCK_RATE_HZ / 4);  
always @(posedge i_clk)  
    counter <= counter + INCREMENT;
```

- After CLOCK\_RATE\_HZ clock edges, the counter will roll over
- The divide by four above, on both numerator and denominator, is just to keep this within 32-bit arithmetic


$$\text{INCREMENT} = \frac{2^{32}}{\text{CLOCK\_RATE\_HZ}}$$

- This is called a *fractional clock divider*
  - The division isn't exact
  - It's often good enough





# Stretch

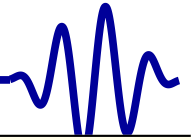


- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- ▷ Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
module stretch(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [26:0]   counter;  
  
    always @(posedge i_clk)  
    if (i_sw)  
        counter <= 0;  
    else if (! (&counter))  
        counter <= counter + 1;  
  
    assign   o_led = !counter[26];  
endmodule
```

FPGA signals are often too fast to see



# Stretch

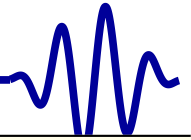

- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- ▷ Stretch
- Too Slow
- Dimmer
- Exercise #1
- Exercise #2


```
module stretch(i_clk, o_led);  
    // ...  
    reg [26:0] counter;  
    always @(posedge i_clk)  
        if (i_sw)  
            counter <= 0;  
        else if (! (&counter))  
            counter <= counter + 1;  
    assign o_led = !counter[26];  
endmodule
```

FPGA signals are often too fast to see

- This slows them down to eye speed
- Only works for a single event though
- Multiple events would overlap, and be no longer distinct



# Too Slow

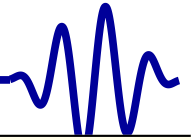

- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- ▷ Too Slow
- Dimmer
- Exercise #1
- Exercise #2

```
module tooslow(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    parameter                                NBITS = 1024;  
    reg      [NBITS-1:0]    counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1;  
  
    assign   o_led = counter[NBITS-1];  
endmodule
```

This is guaranteed to fail a timing check

- It's now time to learn how to check timing
- This design should fail, for reasonable clock speeds



# Dimmer



Can you tell me what this will do?

```
module dimmer(i_clk, o_led);  
    input    wire    i_clk;  
    output   wire    o_led;  
  
    reg      [27:0]   counter;  
  
    always @(posedge i_clk)  
        counter <= counter + 1;  
  
    assign   o_led = (counter[7:0]  
                      < counter[27:20]);  
  
endmodule
```

Lesson Overview  
Registers  
Memoryless Regs  
Flip Flops  
Blocking  
All in Parallel  
Feedback  
Blinky  
Broken Blinky  
Verilator  
Verilator  
Verilator  
Parameters  
Sim Result  
Trace Generation  
GTKWave  
Strobe  
Toggled  
PPS  
Stretch  
Too Slow  
▷ Dimmer  
Exercise #1  
Exercise #2



# Exercise #1



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- ▷ Exercise #1
- Exercise #2

## The walking LED

- Required hardware: 4+ LED's
- Implement blinky, where:
  - Only one LED is ever on at a time
  - The LED that is on moves back and forth



# Exercise #2



- Lesson Overview
- Registers
- Memoryless Regs
- Flip Flops
- Blocking
- All in Parallel
- Feedback
- Blinky
- Broken Blinky
- Verilator
- Verilator
- Verilator
- Parameters
- Sim Result
- Trace Generation
- GTKWave
- Strobe
- Toggled
- PPS
- Stretch
- Too Slow
- Dimmer
- Exercise #1
- ▷ Exercise #2

## Knight Rider's LEDs

- Cause the walking LED to fade rather than turn off
- The LED should be (roughly) off by the time it is turned on again