



Gisselquist
Technology, LLC

1. Wires

Daniel E. Gisselquist, Ph.D.





Lesson Overview



▷ Lesson Overview

First design
Schematic
Constraints
Build the design
First Success!
Simulation
Verilator Driver
Bus Signals
Internal Signals
Schematic
Circular Logic
Sim Result
Examples
Examples

- What is a **wire**?
- What can I do with it?
- How do I build a design?

Objectives

- To get an initial, basic familiarization with combinational logic
- To learn how to run the tools to build a design
- To get an initial design running on an FPGA board



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input    wire    i_sw;  
    output   wire    o_led;  
  
    assign   o_led = i_sw;  
endmodule
```



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input    wire    i_sw;  
    output   wire    o_led;  
  
    assign   o_led = i_sw;  
endmodule
```

- Verilog files contain modules
- This module is named thruwire
- While Verilog allows more than one module per file, I recommend only one module per file.



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input    wire    i_sw;  
    output   wire    o_led;  
  
    assign   o_led = i_sw;  
endmodule
```

- The **module** keyword marks the beginning
- **endmodule** marks the end of the module



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input  wire i_sw;  
    output wire o_led;  
  
    assign o_led = i_sw;  
endmodule
```

- This module declare two ports, `i_sw` and `o_led`
- The first is declared to be an **input**
- The second an **output**
- Both are **wire**'s, but we'll get to that later



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input    wire    i_sw;  
    output   wire    o_led;  
  
    assign   o_led = i_sw;  
  
endmodule
```

- Our one piece of logic sets o_led to be the same as i_sw



First design



Lesson Overview

▷ First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's build a simple Verilog design

```
module thruwire(i_sw, o_led);  
    input    wire    i_sw;  
    output   wire    o_led;  
  
    assign   o_led = i_sw;  
endmodule
```

FPGA's are commonly used as:


- Traffic cops
A programmable/adjustable wire fabric
- Voltage level shifters
- This logic would be appropriate for each
- It generates a simple "wire" through the chip



Schematic



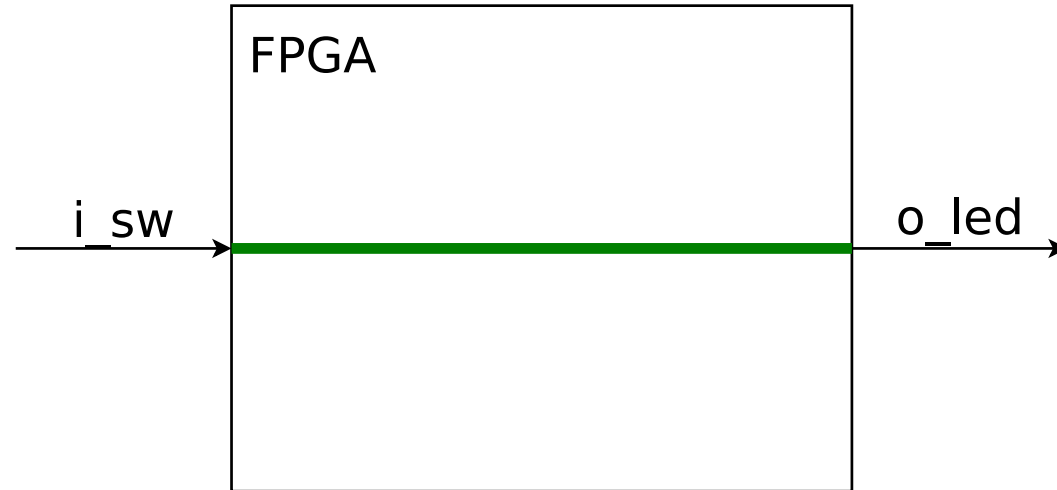Here's what a schematic of this design would look like



All from this assign statement

```
assign    o_led = i_sw;
```

Lesson Overview

First design

▷ Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples



PCF File



If you are using nextpnr, you'll need to create a PCF file

```
set_io  i_sw      P13
set_io  o_led     C8
```

- Maps top-level ports to pins
- You'll find P13 and C8 on the schematic
 - Find the FPGA pins connected to the switch
 - ... and the LED output
 - If your design has no switches, you can use buttons for now
 - Buttons have nasty consequences, but we'll get to that later



UCF File



If you are using ISE, you'll need to create a UCF file

```
NET "i_sw" LOC = "P9" | IOSTANDARD = LVCMOS33;  
NET "o_led" LOC = "N3" | IOSTANDARD = LVCMOS33;
```

- This would be for the older Xilinx FPGA's
- Make sure you actually look up the correct pins
- P13 for one board might be something else on another
On this board, the switch is on pin P9
- Most development boards use the 3.3V LVCMOS standard
You should know if your board is different



XDC File



Lesson Overview

First design

Schematic

▷ Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

If you are using Vivado, you'll need to create a UCF file

```
set_property -dict {PACKAGE_PIN E22
                    IOSTANDARD LVCMOS12} [get_ports {i_sw}]
set_property -dict {PACKAGE_PIN T14
                    IOSTANDARD LVCMOS25} [get_ports {o_led}]
```

- This would be for the newer Xilinx FPGA's
- Usually, the vendor will provide a "master XDC" file
- From there, you should be able to
 - Rename the ports to `i_sw` and `o_led`
 - Comment out every other I/O port



Build the design



Lesson Overview

First design

Schematic

Constraints

▷ Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

For an iCE40 design, this will look like:

```
% yosys -p 'synth_ice40 -json thruwire.json' \  
    thruwire.v  
% nextpnr-ice40 --hx8k --package ct256 \  
    --pcf thruwire.pcf --json thruwire.json  
% icepack thruwire.asc thruwire.bin
```

You'll need to do this for every project—get used to this flow.

- A makefile can drastically simplify this process

You should now have a file `thruwire.bin` that you can load onto your board.

- If you aren't using an iCE40, follow your chip vendor's instructions



First Success!



- Lesson Overview
- First design
- Schematic
- Constraints
- Build the design
- ▷ First Success!
- Simulation
- Verilator Driver
- Bus Signals
- Internal Signals
- Schematic
- Circular Logic
- Sim Result
- Examples
- Examples

Follow your board vendor's instructions for loading this file onto your board.

Notice now that every time you flip the switch, the LED responds



First Success!



- Lesson Overview
- First design
- Schematic
- Constraints
- Build the design
 - ▷ First Success!
- Simulation
- Verilator Driver
- Bus Signals
- Internal Signals
- Schematic
- Circular Logic
- Sim Result
- Examples
- Examples

Follow your board vendor's instructions for loading this file onto your board.

Notice now that every time you flip the switch, the LED responds Yaaaayyyyyy!!! Your first FPGA design.



Simulation



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

▷ Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Simulation is an important part of design

Simulation	Hardware
Can trace all signals	Can only see some signals
Extended tests cost GB	Extended tests are simple
Easy to debug	Hard to debug

hardware is so hard to debug, simulation is vital

Because

- A successful complex project
... *requires simulation!*



Verilator



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

▷ Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Let's now build our design using Verilator

```
% verilator -Wall -cc thruwire.v
% cd obj_dir/
% make -k Vthruwire.mk
```

- Verilator compiles Verilog into C++ placed into obj_dir/
- The make command then builds this converted C++ file into a shared object file we can now use



Verilator Driver



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

▷ Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

You'll need a main simulation driver too.

```
#include <stdio.h>
#include <stdlib.h>
#include "Vthruwire.h"
#include "verilator.h"

int main(int argc, char **argv) {
    // Your logic here
}
```



Verilator Driver



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

▷ Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

You'll need a main simulation driver too.

```
// ...  
int main(int argc , char **argv) {  
    // Call commandArgs first!  
    Verilated::commandArgs(argc , argv);  
  
    // Create our design  
    Vthruwire *tb = new Vthruwire;  
  
    // ...  
}
```



Verilator Driver



You'll need a main simulation driver too.

```
int main(int argc, char **argv) {  
    // ...  
  
    // Now run the design thru 20 timesteps  
    for(int k=0; k<20; k++) {  
        // We'll set the switch input  
        // to the LSB of our counter  
        tb->i_sw = k&1;  
  
        tb->eval();  
  
        // ...  
    }  
}
```



Verilator Driver



You'll need a main simulation driver too.

```
int main(int argc, char **argv) {  
    // ...  
    for(int k=0; k<20; k++) {  
        // ...  
        // LSB of our counter  
        tb->i_sw = k&1;  
  
        tb->eval();  
  
        // Now let's print our results  
        printf("k_=%2d, ", k);  
        printf("sw_=%d, ", tb->i_sw);  
        printf("led_=%d\n", tb->o_led);  
    }  
}
```

Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

▷ Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples



Building it all



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

▷ Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

Last step, let's put it all together:

```
% g++ -I /usr/share/verilator/include \
% /usr/share/verilator/include/verilated.cpp \
% obj_dir/Vthruwire__ALL.a \
% thruwire.cpp -o thruwire
```

Wow, that's pretty complicated.

You should have a Makefile in your ex-01-thruwire directory with both the code and the build instructions.

```
% cd ex-01-thruwire/
% make
# (Make output skipped for brevity)
%
```



Simulation



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

▷ Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

We can now run our simulator!

```
% thruwire
k = 0, sw = 0, led = 0
k = 1, sw = 1, led = 1
k = 2, sw = 0, led = 0
k = 3, sw = 1, led = 1
k = 4, sw = 0, led = 0
k = 5, sw = 1, led = 1
k = 6, sw = 0, led = 0
k = 7, sw = 1, led = 1
k = 8, sw = 0, led = 0
k = 9, sw = 1, led = 1
# .... (Lines skipped for brevity)
%
```



Bus Signals



That was one single wire. We can also declare values consisting of many bits.

```
input  wire [8:0] i_sw;  
output wire [8:0] i_o_led;
```

This defines

- `i_sw` to be 9-input wires, and
- `o_led` to be 9-output wires



Internal Signals



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

▷ Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

You can also declare and work with internal wires

```
wire      [8:0]    w_internal;
```

These wires can now be used in logic

```
assign    w_internal = 9'h87;  
assign    o_led = i_sw ^ w_internal;
```



Literals



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

▷ Internal Signals

Schematic

Circular Logic

Sim Result

Examples

Examples

A Verilog literal is defined as

- A width
- An apostrophe
- A numeric type: h, d, o, b, sd
- The value: a series of digits, possibly containing underscores

Examples include:

1'b0 1'b1 2'b01 4'b0101 4'h5 -7'sd124 32'hdead_beef



Operators



Lesson Overview

First design
Schematic
Constraints
Build the design
First Success!
Simulation
Verilator Driver
Bus Signals
▷ Internal Signals
Schematic
Circular Logic
Sim Result
Examples
Examples

The Verilog language supports the following operators

+	Addition	—	Subtraction
<<	Left Shift	>>	Right shift
—	Unary negation	?:	Tertiary operator
~	Bit-wise negation	^	Bit-wise XOR
	Bitwise OR	&	Bitwise AND
	Logical OR	&&	Logical and
!	Logical negation	>>>	Arithmetic right shift
==	Equality	!=	Inequality
<, <=	Less than (Equal)	>, >=	Greater than (Equal)
Limited, use with care		Avoid within logic	
*	Multiplication	/	Division
		%	Remainder

- Some FPGA's support native multiplication
- None support a single clock divide



Schematic




Lesson Overview
First design
Schematic
Constraints
Build the design
First Success!
Simulation
Verilator Driver
Bus Signals
Internal Signals
▷ Schematic
Circular Logic
Sim Result
Examples
Examples

From this code:

```
assign    w_internal = 9'h87;  
assign    o_led = i_sw ^ w_internal;
```

Get this internal structure:

 




Circular Logic



Avoid circular logic!

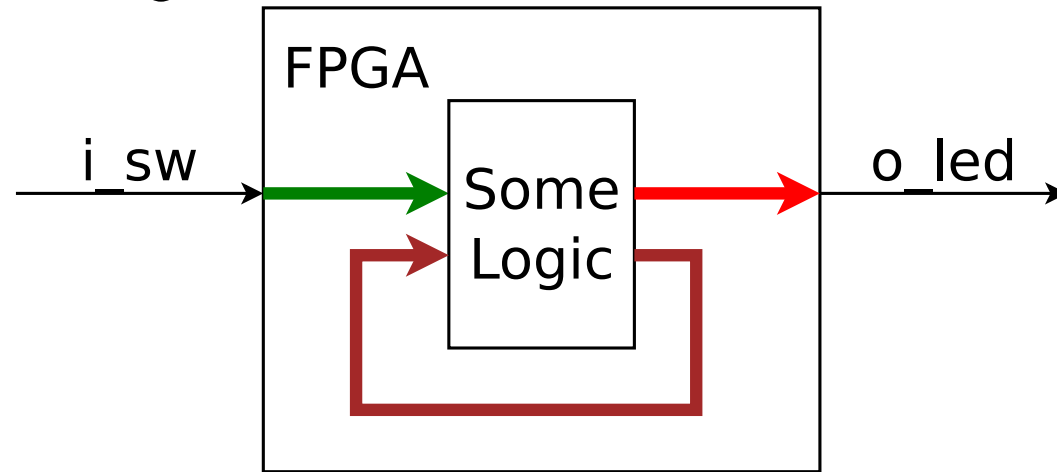

Example:

```
assign    o_led = i_sw + o_led;
```

- ❑ This doesn't work in hardware like it did in Software
- ❑ This is roughly equivalent to creating a short circuit
- ❑ Most tools will fail to build such designs



Updated Driver



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

▷ Circular Logic

Sim Result

Examples


Examples

Let's update our driver for this wire bus design

```
int main(int argc , char **argv) {  
    // ...  
    for(int k=0; k<20; k++) {  
        // ...  
        // Bottom 9 bits of counter  
        tb->i_sw = k&1ff;  
  
        tb->eval();  
  
        // Now let's print our results  
        printf("k_=%2d, ", k);  
        printf("sw_=%3x, ", tb->i_sw);  
        printf("led_=%3x\n", tb->o_led);  
    }  
}
```



Sim Result

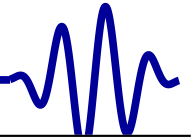

- Lesson Overview
- First design
- Schematic
- Constraints
- Build the design
- First Success!
- Simulation
- Verilator Driver
- Bus Signals
- Internal Signals
- Schematic
- Circular Logic
- ▷ Sim Result
- Examples
- Examples

```
% ./maskbus
k = 0, sw = 0, led = 87
k = 1, sw = 1, led = 86
k = 2, sw = 2, led = 85
k = 3, sw = 3, led = 84
k = 4, sw = 4, led = 83
k = 5, sw = 5, led = 82
k = 6, sw = 6, led = 81
k = 7, sw = 7, led = 80
k = 8, sw = 8, led = 8f
k = 9, sw = 9, led = 8e
# .... (Lines skipped for brevity)
%
```



Examples




Lesson Overview
First design
Schematic
Constraints
Build the design
First Success!
Simulation
Verilator Driver
Bus Signals
Internal Signals
Schematic
Circular Logic
Sim Result
▷ Examples
Examples

What can you do with wires and wire logic?

 Example: Multiplexer

```
input    wire    i_a, i_b, i_sel;  
output   wire    o_out;  
  
assign   o_out = (i_sel) ? i_a : i_b;
```





Examples



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

▷ Examples

What can you do with wires and wire logic?

Example: Multiplexer

```
input      wire      i_a, i_b, i_sel;  
output     wire      o_out;  
  
assign     o_out = (i_sel) ? i_a : i_b;
```

- This is a good example of the tertiary operator
- Interested in making a connection to one of two serial ports?
- How about connecting one of two bus masters to an interconnect?

We'll get to this later.



Examples




Lesson Overview
First design
Schematic
Constraints
Build the design
First Success!
Simulation
Verilator Driver
Bus Signals
Internal Signals
Schematic
Circular Logic
Sim Result
Examples
▷ Examples

What can you do with wires and wire logic?

 Example: Parity check

```
input    wire    [7:0]    i_word;  
output   wire                   o_parity;  
  
assign   o_parity = ^i_word;
```





Examples



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

▷ Examples

What can you do with wires and wire logic?

Example: Parity check

```
input  wire [7:0] i_word;
output wire      o_parity;

assign o_parity = ^i_word;
```

This form of XOR is a *reduction operator*

- It XORs all the word's bits together
- Other reduction operators include | and &



Examples



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

▷ Examples

What can you do with wires and wire logic?

Example: Interrupt detector

```
input    wire    [7:0]    i_irq_source;  
output   wire    o_irq;  
  
assign   o_irq = | i_irq_source;
```

- i_irq_source contains eight interrupt sources
- o_irq is true if any interrupt source is true



Examples



- Lesson Overview
- First design
- Schematic
- Constraints
- Build the design
- First Success!
- Simulation
- Verilator Driver
- Bus Signals
- Internal Signals
- Schematic
- Circular Logic
- Sim Result
- Examples
 - ▷ Examples

What can you do with wires and wire logic?

Example: CPU stall determination

```
assign    dcd_stall = (dcd_valid)&&(op_stall);
```

From the ZipCPU, the decode stage must stall if

- It has produced a valid result, and
 - The next stage, read operands, is stalled for some reason
- Read operands might be stalled if the ALU is stalled
- These stalls can back up through the CPU



Examples



Lesson Overview

First design

Schematic

Constraints

Build the design

First Success!

Simulation

Verilator Driver

Bus Signals

Internal Signals

Schematic

Circular Logic

Sim Result

Examples

▷ Examples

What can you do with wires and wire logic?

Example: Determining if there's a phase error in a phase lock loop

```
assign phase_err = (output_phase != input_phase);
```

In this case, the loop will adjust if there are any errors