



Gisselquist
Technology, LLC

4. Pipeline Control

Daniel E. Gisselquist, Ph.D.





Lesson Overview



▷ Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

Objectives

- State diagrams
- Pipeline control structures
- Minimal peripherals
- Simulating Wishbone
- **\$past()** operator
- Verifying Wishbone



LED Walker



Lesson Overview

▷ LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus


Conclusion

Let's make our LED's walk on command

- Bus requests
- State Diagram



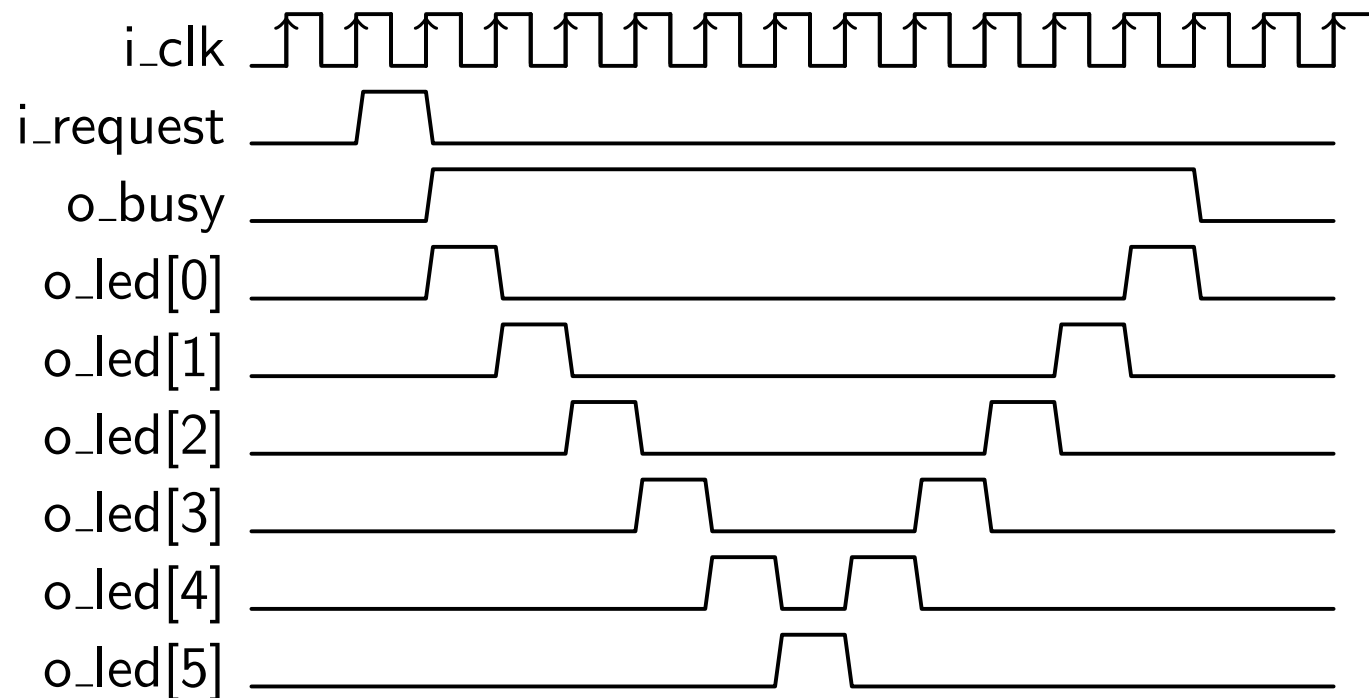Let's adjust our LED sequence to require a request




- Our goal will be to create a design with these outputs
- If successful, you'll see this in GTKwave



Goal



We'll add state ID's to this diagram

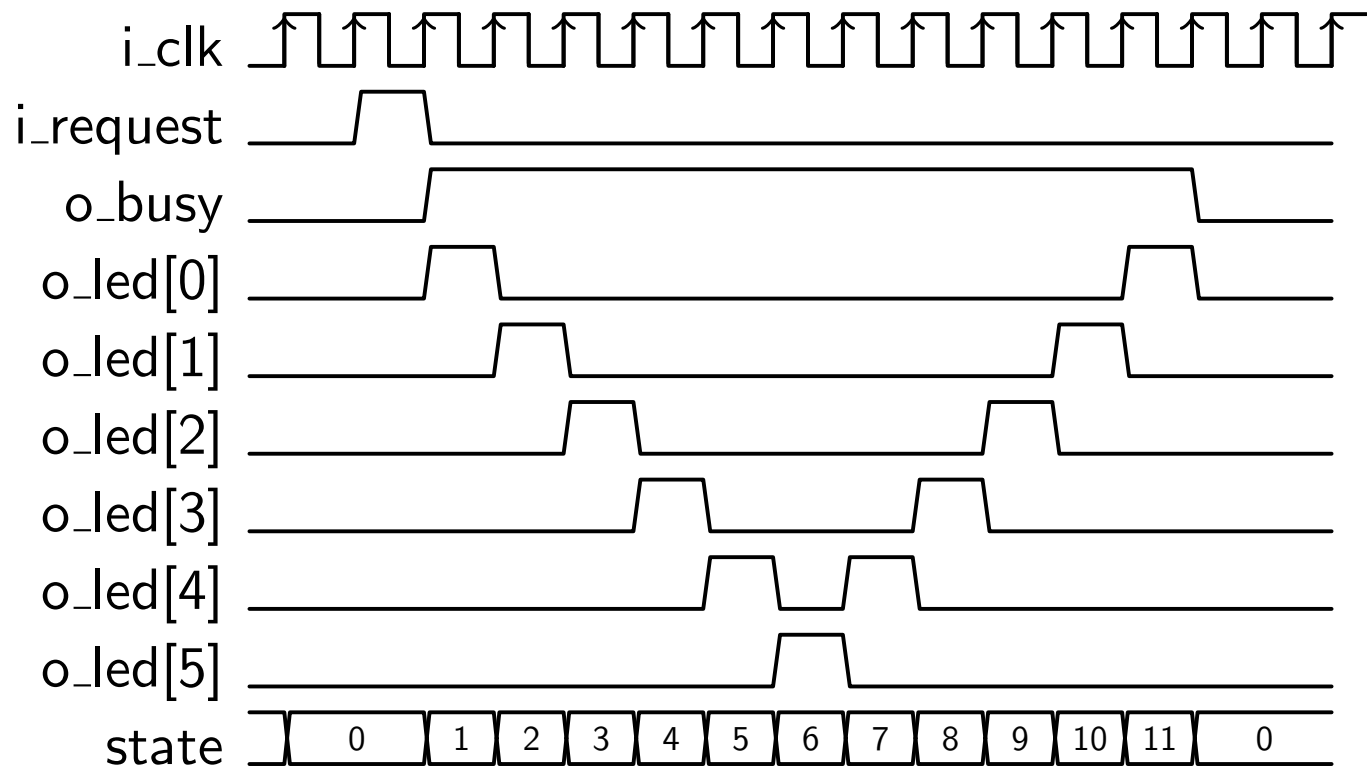

- Our goal will be to create a design with these outputs
- If successful, you'll see this in GTKwave



State Transition



Lesson Overview

▷ LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

The key to this design is the idle state


- The design waits in state 0 for an `i_request`
- Only responds when it isn't busy

```
initial state = 0;
always @(posedge i_clk)
if ((i_request)&&(!o_busy))
    state <= 4'h1;
else if (state >= 4'hB)
    state <= 4'h0;
else if (state != 0)
    state <= state + 1'b1;

assign o_busy = (state != 0);
```



State Transition Diagrams

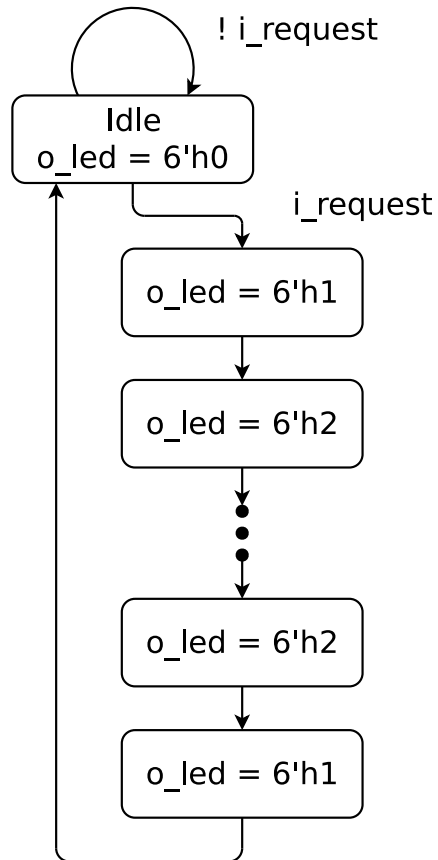

- States
 - Shown as named bubbles
 - Moore FSM: states include outputs
This FSM is a Moore FSM
- Transitions
 - Arrows between states
 - May contain transition criteria
 - Mealy FSM: transitions include outputs



Outputs



Lesson Overview

LED Walker

▷ Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

We can use a **case** statement for our outputs

```
always @(posedge i_clk)
case(state)
4'h1: o_led <= 6'b00_0001;
4'h2: o_led <= 6'b00_0010;
4'h3: o_led <= 6'b00_0100;
4'h4: o_led <= 6'b00_1000;
4'h5: o_led <= 6'b01_0000;
4'h6: o_led <= 6'b10_0000;
4'h7: o_led <= 6'b01_0000;
// ...
4'ha: o_led <= 6'b00_0010;
4'hb: o_led <= 6'b00_0001;
default: o_led <= 6'b00_0000;
endcase
```

Or can we? Does this work?



Pipeline Strategies



- Lesson Overview
- LED Walker
- Diagrams
 - ▷ Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Several approaches to pipeline logic

1. Apply the logic on every clock

```
// From the PPS-II implementation  
always @(posedge i_clk)  
    counter <= counter + INCREMENT;
```



Pipeline Strategies



- Lesson Overview
- LED Walker
- Diagrams
 - ▷ Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Several approaches to pipeline logic

1. Apply the logic on every clock
2. Wait for a clock enable (CE) signal

```
// From the Integer Clock Divider
always @(posedge i_clk)
if (stb) // this would be the CE signal
begin
    if (led_index >= 4'd13)
        led_index <= 0;
    else
        led_index <= led_index + 1'b1;
end
```



Pipeline Strategies



- Lesson Overview
- LED Walker
- Diagrams
 - ▷ Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion


Several approaches to pipeline logic

1. Apply the logic on every clock
2. Wait for a clock enable (CE) signal
3. Move on a request, but only when not busy


```
// Today's logic: Wait for the request
always @(posedge i_clk)
if ((i_request)&&(!o_busy))
    state <= 4'h1;
else if (state >= 4'hB)
    state <= 4'h0;
else if (state != 0)
    state <= state + 1'b1;
```

Above: A mix of pipeline and state machine logic

This is fairly common

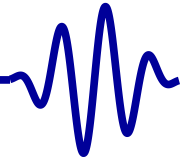

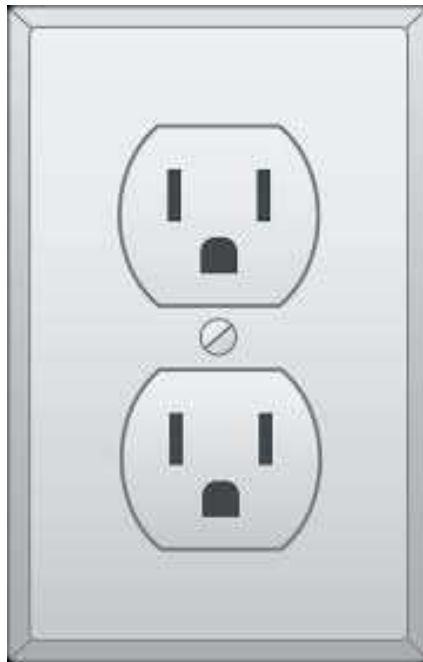Interface standards simplify plugging things in




A bus interface can be standardized

- A master makes requests
A slave responds
- Read request
 - Contains an address
 - Slave responds with a value
- Write request
 - Contains an address
 - Contains a value
 - Slave responds with an acknowledgment




Bus Topology

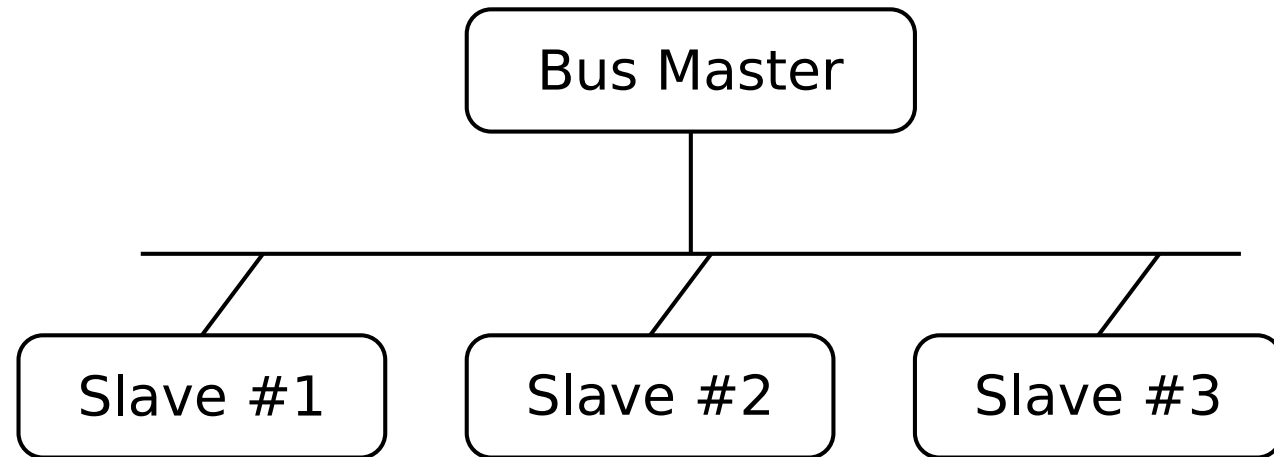


- Every bus has a master
- A Bus may have many slaves
Slaves are differentiated by their address
- All connected via an *interconnect*
- A slave on one bus may be a master on another




There are many bus standards

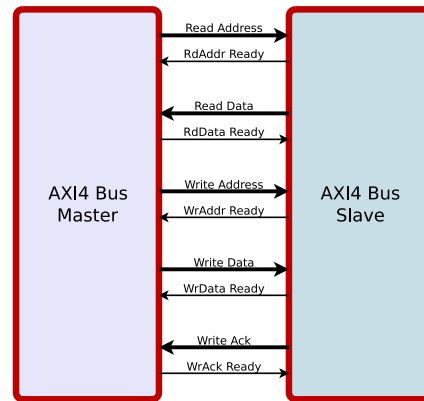

AXI

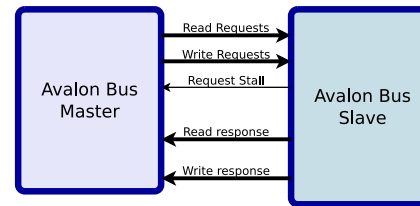

Avalon

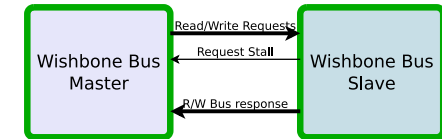

Wishbone

I like Wishbone for its simplicity


- Only one request channel
AXI has three, Avalon has two
- Only the request channel can stall
- Acknowledgements are simple



Wishbone Bus



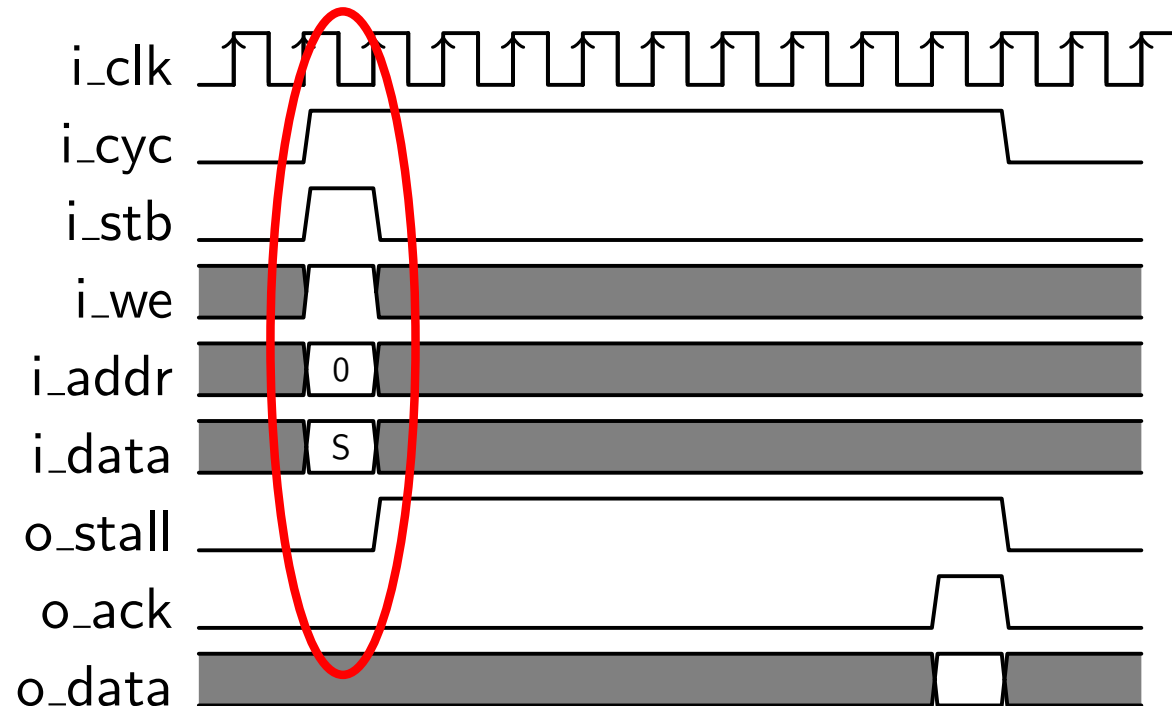I use [Wishbone B4](#), pipelined mode exclusively




- A request takes place any time $(i_stb) \& \& (!o_stall)$
Just like our $(i_request) \& \& (!o_busy)$
- The request details are found in i_we , i_addr , and i_data
- These wires are don't care if $(i_stb) \& \& (!o_stall)$ isn't true



Wishbone Bus



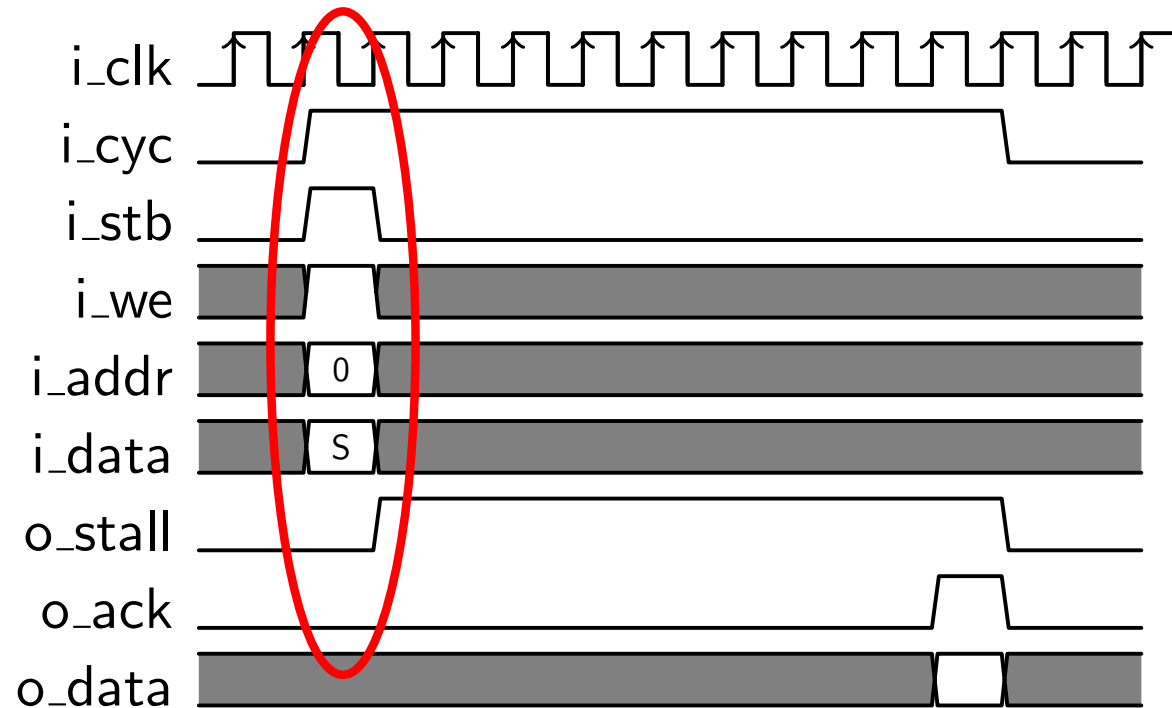I use [Wishbone B4](#), pipelined mode exclusively




- If `i_we`, this is a write request
- A write request writes `i_data` to address `i_addr`
- Read requests ignore `i_data`



Wishbone Bus



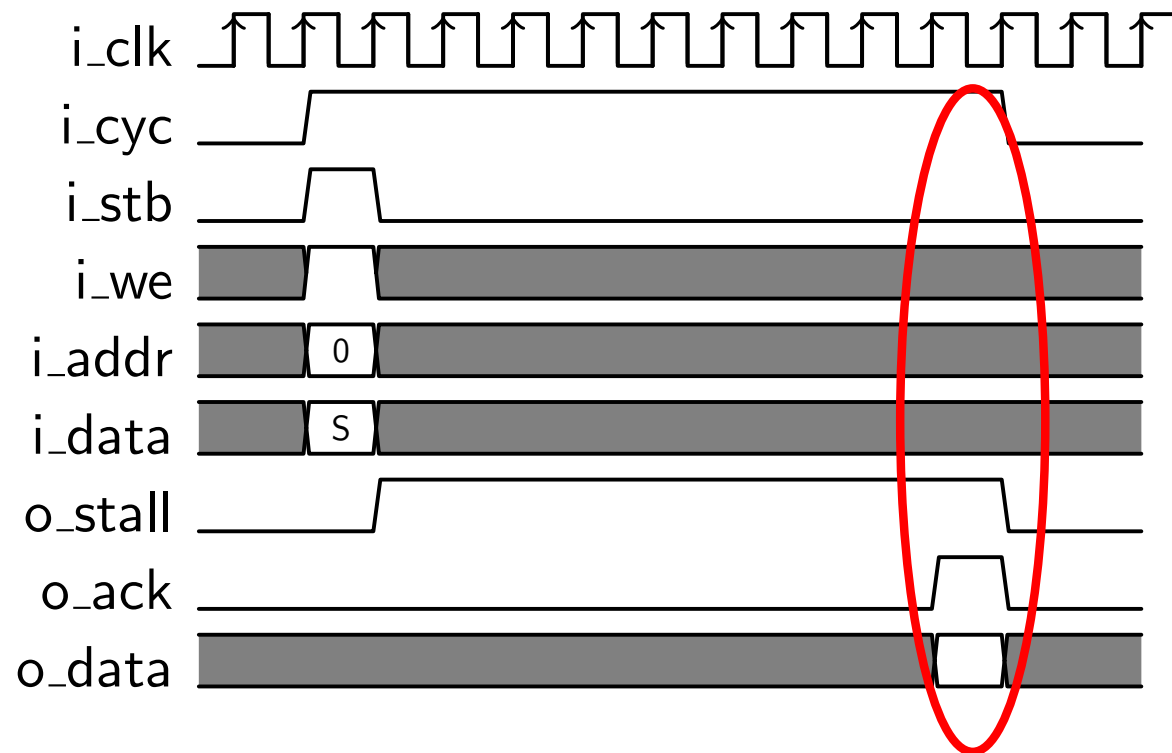I use [Wishbone B4](#), pipelined mode exclusively



- The response is signaled when o_ack is true
- If this was a read request, o_data would have the result




Wishbone Bus



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
 - ▷ Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

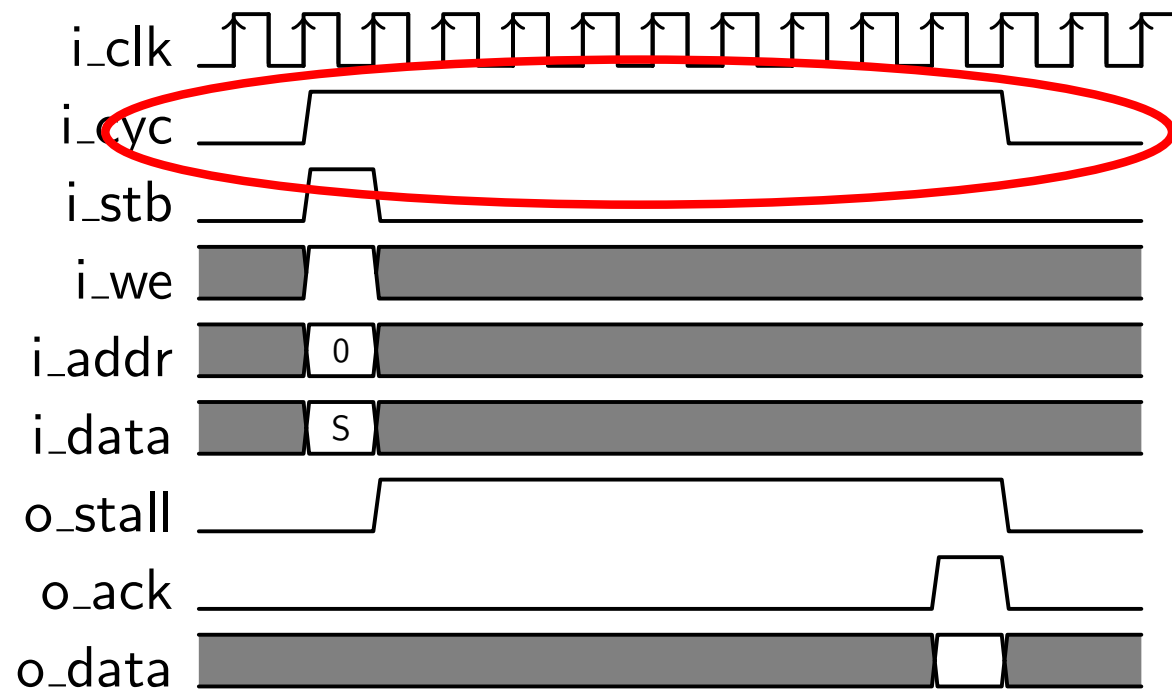I use [Wishbone B4](#), pipelined mode exclusively




- `i_cyc` will be true from request to ack
- `i_stb` will never be true unless `i_cyc`



Wishbone Bus



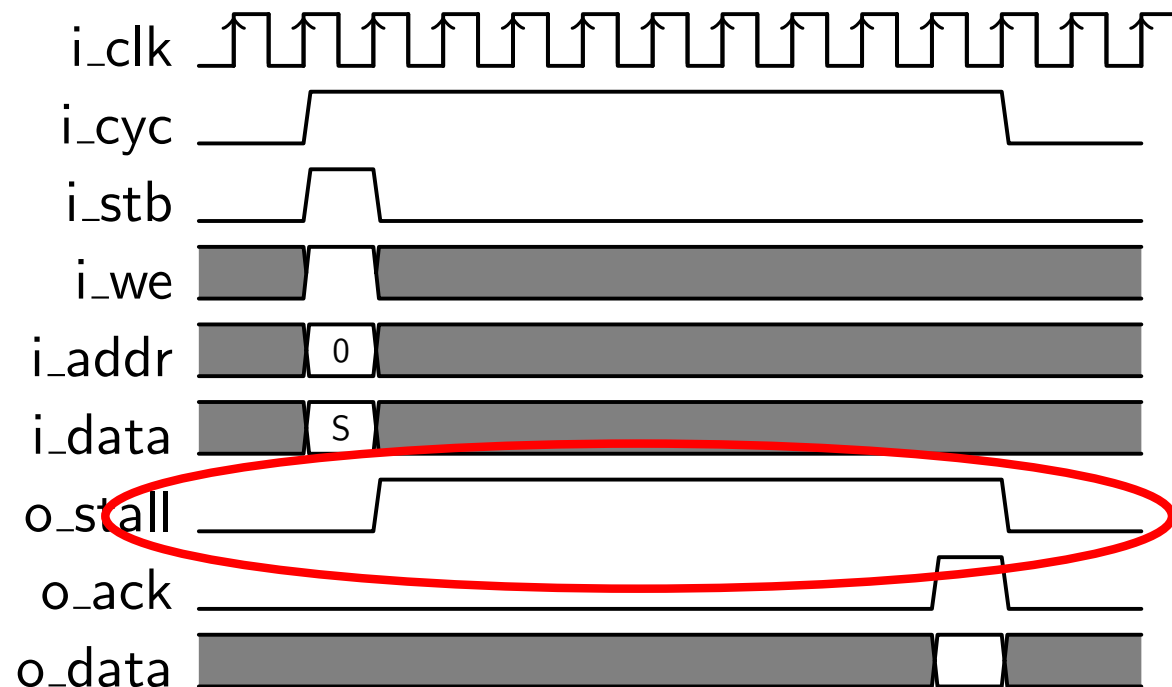I use [Wishbone B4](#), pipelined mode exclusively



- A slave must respond to every request
- Multiple requests can be made before the slave responds
- This is controlled by the `o_stall` signal



Wishbone Bus



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- ▷ Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Let's **Wishbone enable** our core

- We'll start the LED cycling on a write
- Writes will stall if the LED's are busy
- Return our state on a read
- We'll also acknowledge all requests immediately



Wishbone Bus



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- ▷ Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

- We'll immediately acknowledge any transaction

```
initial o_ack = 1'b0;  
always @(posedge i_clk)  
    o_ack <= (i_stb)&&(!o_stall);
```

- Stall if we're busy and another cycle is requested


```
assign o_stall = (busy)&&(i_we);
```

- Return state upon any read

```
assign o_data = { 28'h0, state };
```



Simulation

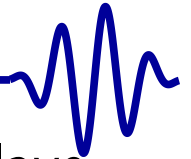

- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
 - ▷ Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

It helps to be able to communicate with your wishbone slave during simulation

- Makes simulations easier
- Transaction scripting makes more sense
- Just need to implement two functions

- One to read from the bus

```
unsigned          wb_read(unsigned a);
```


- One to write to the bus

```
void          wb_write(unsigned a, unsigned v);
```

- We'll come back later and create high-throughput versions of these



Sim Read

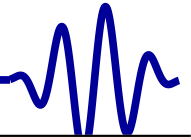


- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- ▷ Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

```
unsigned wb_read(unsigned a) {  
    tb->i_cyc = tb->i_stb = 1;  
    tb->i_we   = 0;  
    tb->i_addr = a;  
  
    // Make the read request  
    while(tb->o_stall)  
        tick(tb);  
    tick(tb);  
    tb->i_stb = 0;  
    // Wait for the ACK  
    while(!tb->o_ack)  
        tick(tb);  
    // Idle the bus, and read the response  
    tb->i_cyc = 0;  
    return tb->o_data;  
}
```



Sim Write

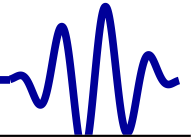

- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- ▷ Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

```
void wb_write(unsigned a, unsigned v) {  
    tb->i_cyc = tb->i_stb = 1;  
    tb->i_we   = 1;  
    tb->i_addr = a;  
    tb->i_data = v;  
    // Make the write request  
    while(tb->o_stall)  
        tick(tb);  
    tick(tb);  
    tb->i_stb = 0;  
    // Wait for the acknowledgement  
    while(!tb->o_ack)  
        tick(tb);  
    // Idle the bus and return  
    tb->i_cyc = 0;  
  
}
```




Run Twice



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

▷ Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

This makes building the sim easy!

- Let's tell our LED's to cycle twice

```
int main(int argc, char **argv) {  
    // Setup Verilator (same as before)  
    // Read from the current state  
    printf("Initial state is: 0x%02x\n",  
           wb_read(0));  
    for(int cycle=0; cycle<2; cycle++) {  
        // Wait five clocks  
        for(int i=0; i<5; i++)  
            tick();  
  
        // Start the LEDs cycling  
        wb_write(0,0);  
        tick();  
        // ... (next page)
```



Display State



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

▷ Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

This makes building the sim easy!

- Here's the other half


```
// ... (last page)
while((state = wb_read(0))!=0) {
    if ((state != last_state)
        || (tb->o_led != last_led)) {
        printf(// something useful
              );
    } tick();

    last_state = state;
    last_led = tb->o_led;
}
```

The [full example code](#) is available on line



Unused Logic

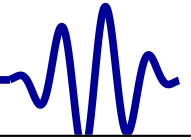

- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
 - ▷ Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

```
% verilator --trace -Wall -cc reqwalker.v
%Warning-UNUSED: reqwalker.v:37:
    Signal is not used: i_cyc
%Warning-UNUSED: reqwalker.v:38:
    Signal is not used: i_addr
%Warning-UNUSED: reqwalker.v:39:
    Signal is not used: i_data
%Error: Exiting due to 3 warning(s)
%Error: Command Failed /usr/bin/verilator_bin
    --trace -Wall -cc reqwalker.v
%
```

What happened?



Unused Logic



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
 - ▷ Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

What happened?

- The `-Wall` flag to Verilator looks for all kinds things you might not have meant
- It turns warnings into errors
- It found logic we weren't using: `i_cyc`, `i_addr`, and `i_data`
 - These are standard bus interface wires
 - I often include them, even if not used, to keep the interface standardized
- So how do get our design to work?



Unused Logic



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
 - ▷ Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Getting Verilator to ignore unused logic

- Use the *// Verilator lint_off UNUSED* command

```
// Verilator lint_off UNUSED
wire    unused;
assign  unused = &{ 1'b0, i_cyc, i_addr, i_data };
// Verilator lint_on  UNUSED
```

- Verilator will now no longer check if unused is used or not



Sim Exercise



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- ▷ Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Build and run the demo

- Examine the trace
- Examine the output


Does it work like you expected?



Trace bias



Look at the trace. Can you explain this?

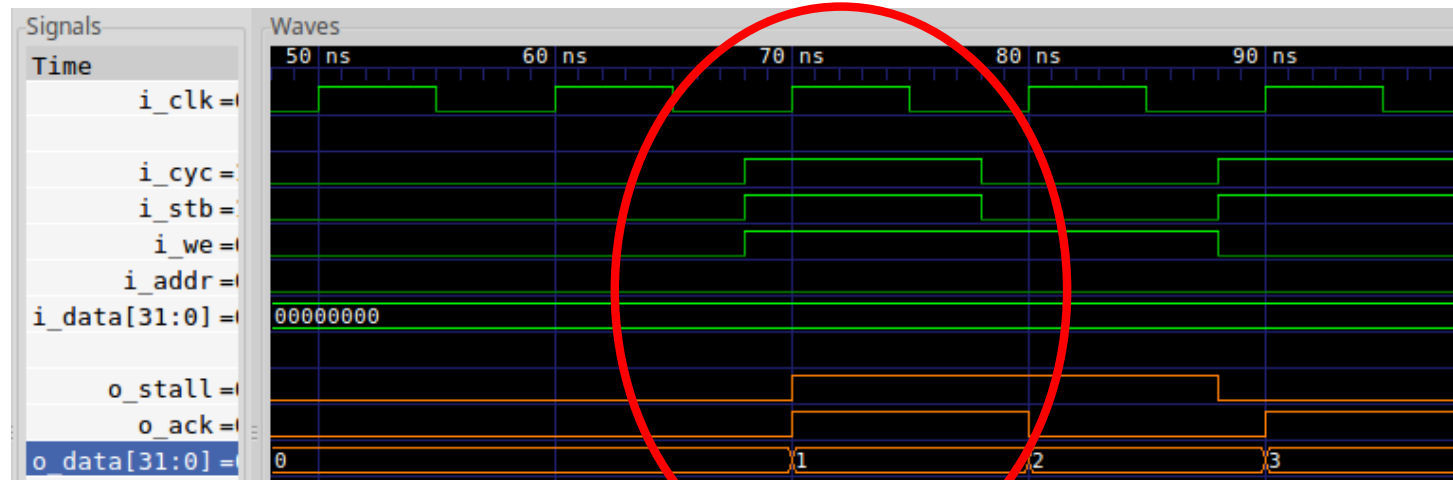

Our inputs aren't clock synchronous!

- Normally, all logic changes on the posedge of i_clk
- i_cyc, i_stb, i_we are changing before the clock



Trace bias



This is a consequence of our `trace()` function

- We set our input values, `i_cyc`, etc *before* calling `tick()`

```
void tick(void) {  
    tickcount++;  
  
    tb->eval(); // Adjusted inputs are  
    if (tfp)    // recorded here  
        tfp->dump(tickcount * 10 - 2);  
  
    tb->i_clk = 1; // <--- posedge i_clk  
    tb->eval();   // takes place here!  
    if (tfp)  
        tfp->dump(tickcount * 10);  
    // ...  
}
```




Trace bias



This is a consequence of our `trace()` function

- We set our input values, `i_cyc`, etc *before* calling `tick()`

```
void tick(void) {  
    tickcount++;  
  
    tb->eval(); // Adjusted inputs are  
    if (tfp)    // recorded here  
        tfp->dump(tickcount * 10 - 2);  
  
    tb->i_clk = 1; // <--- posedge i_clk  
    tb->eval();   // takes place here!  
    if (tfp)  
        tfp->dump(tickcount * 10);  
    // ...  
}
```



Trace bias



This is a consequence of our **trace()** function

- We set our input values, `i_cyc`, etc *before* calling **tick()**

```
void tick(void) {  
    tickcount++;  
  
    tb->eval(); // Adjusted inputs are  
    if (tfp)    // recorded here  
        tfp->dump(tickcount * 10 - 2);  
}
```

- The **tfp->dump(tickcount*10 -2)** dumps the state of everything just before the positive edge of the clock
- This captures the changes made to `i_cyc`, `i_stb`, `i_we`, etc., in **wb_read()** and **wb_write()**
- The trace accurately reflected these changes taking place before the clock edge



Trace bias



This is a consequence of our **trace()** function

- We set our input values, `i_cyc`, etc *before* calling **tick()**
- Had we done otherwise, combinatorial logic wouldn't have settled before **posedge** `i_clk`
- Worse, the trace wouldn't make any sense
- This way, things work. Logic matches the trace. It just looks strange.



Simulation output



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- ▷ Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion


Is this an output you expected?

```
% ./reqwalker
Initial state is: 0x00
    10: State # 4  --0---
    12: State # 6  ----0-
    14: State # 8  ----0-
    16: State #10  --0---
    27: State # 4  --0---
    29: State # 6  ----0-
    31: State # 8  ----0-
    33: State #10  --0---
%
```

Let's look at the trace again!



Look at the trace. Can you explain this?

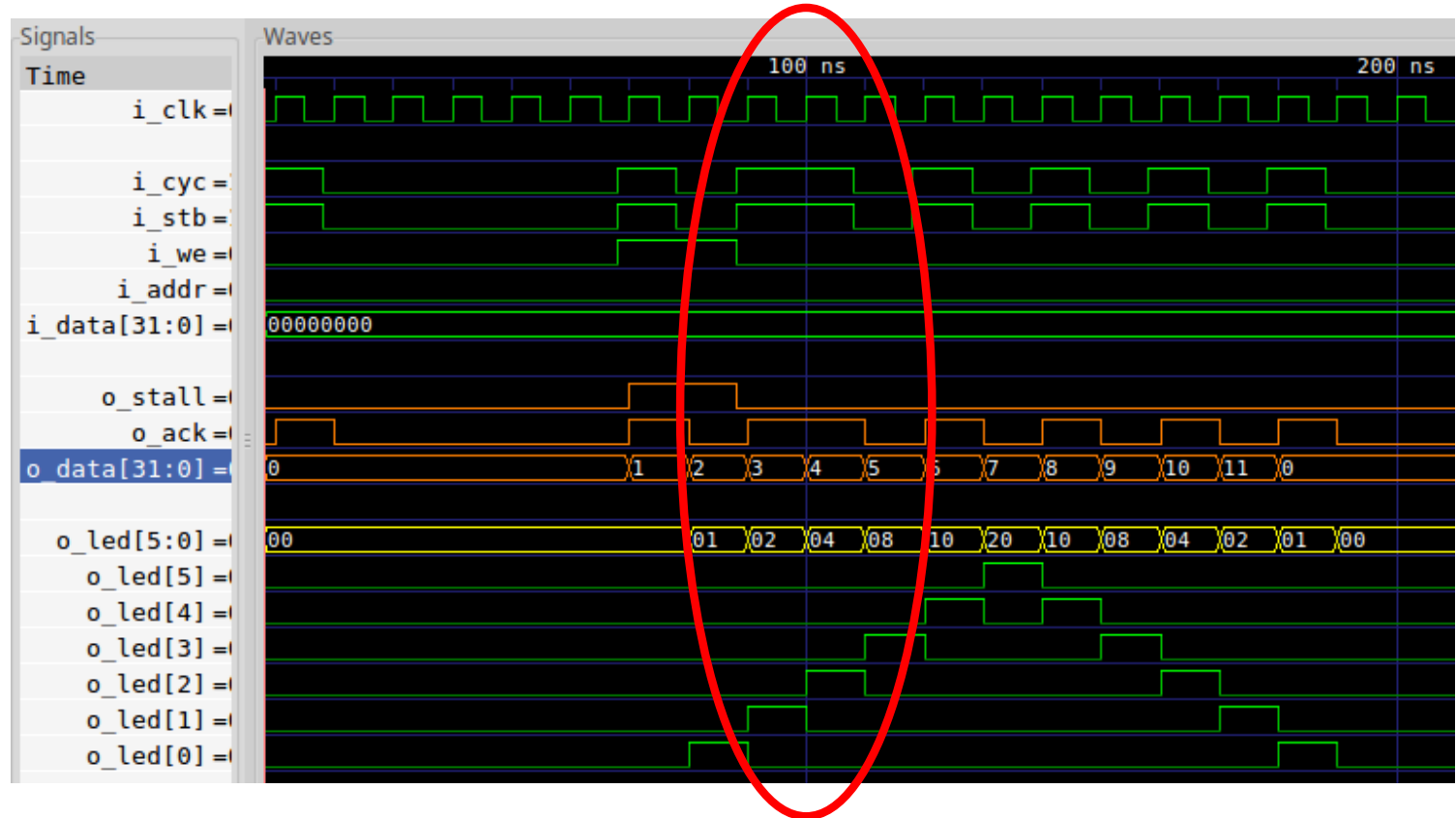


- Why are we getting two acks in a row?
- We never created two adjacent requests!



Double ACKs



Look at the trace. Can you explain this?

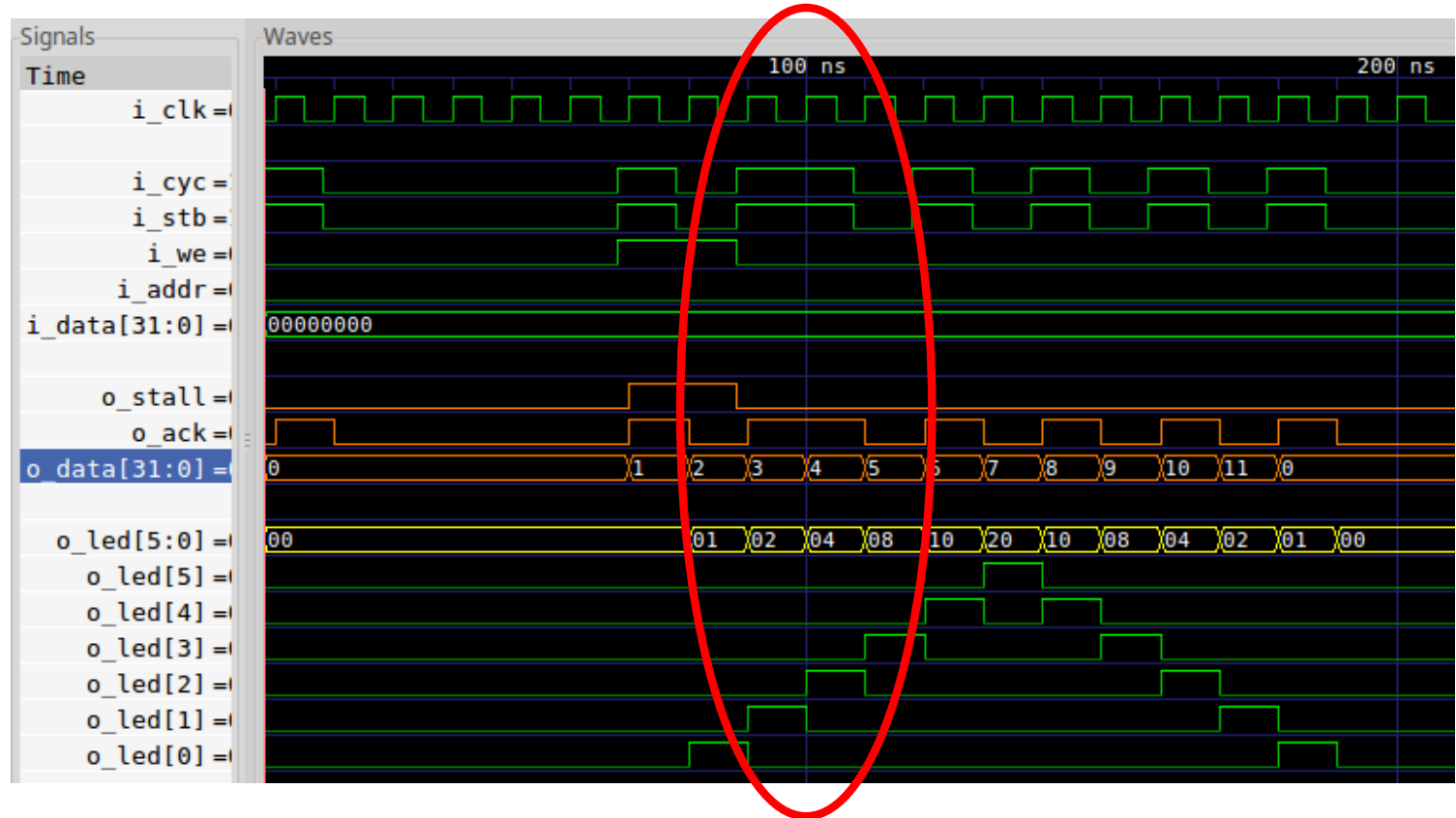

- The stall line depends upon i_we
- Without a call to **tb->eval()**, it won't update!



Double ACKs



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- ▷ Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

Remember how we defined `o_stall`?

```
assign o_stall = (busy)&&(i_we);
```

- **wb_write()** and **wb_read()** both adjust `i_we`
- ... without calling Verilator to give it a chance to update `o_stall` before referencing it!
- `o_stall` is still updated before the clock, but not until after we used it in **wb_write()** and **wb_read()**
- We can fix this by calling **tb->eval()** to get Verilator to adjust `o_stall`



Double ACKs



Need to call **tb->eval()**

- o_stall depends upon a Verilator input, i_we
 - Fixing this requires an extra call to **eval()**
 - I don't normally need to do this
- Both **wb_read()** and **wb_write()** need to be updated
- Example update to **wb_read()**:

```
unsigned wb_read(unsigned a) {  
    tb->i_cyc = tb->i_stb = 1;  
    tb->i_we   = 0; tb->eval();  
    tb->i_addr = a;  
    // Make the request  
    // ...  
}
```




Exercise



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- ▷ Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion


Rebuild and run again. Is this better?

```
% ./reqwalker
Initial state is: 0x00
      9: State # 3 -0-----
     11: State # 5 ---0---
     13: State # 7 -----0
     15: State # 9 ---0---
     17: State #11 -0-----
     27: State # 3 -0-----
     29: State # 5 ---0---
     31: State # 7 -----0
     33: State # 9 ---0---
     35: State #11 -0-----
%
```

But, why are we reading every other trace?



Look at the ACK's

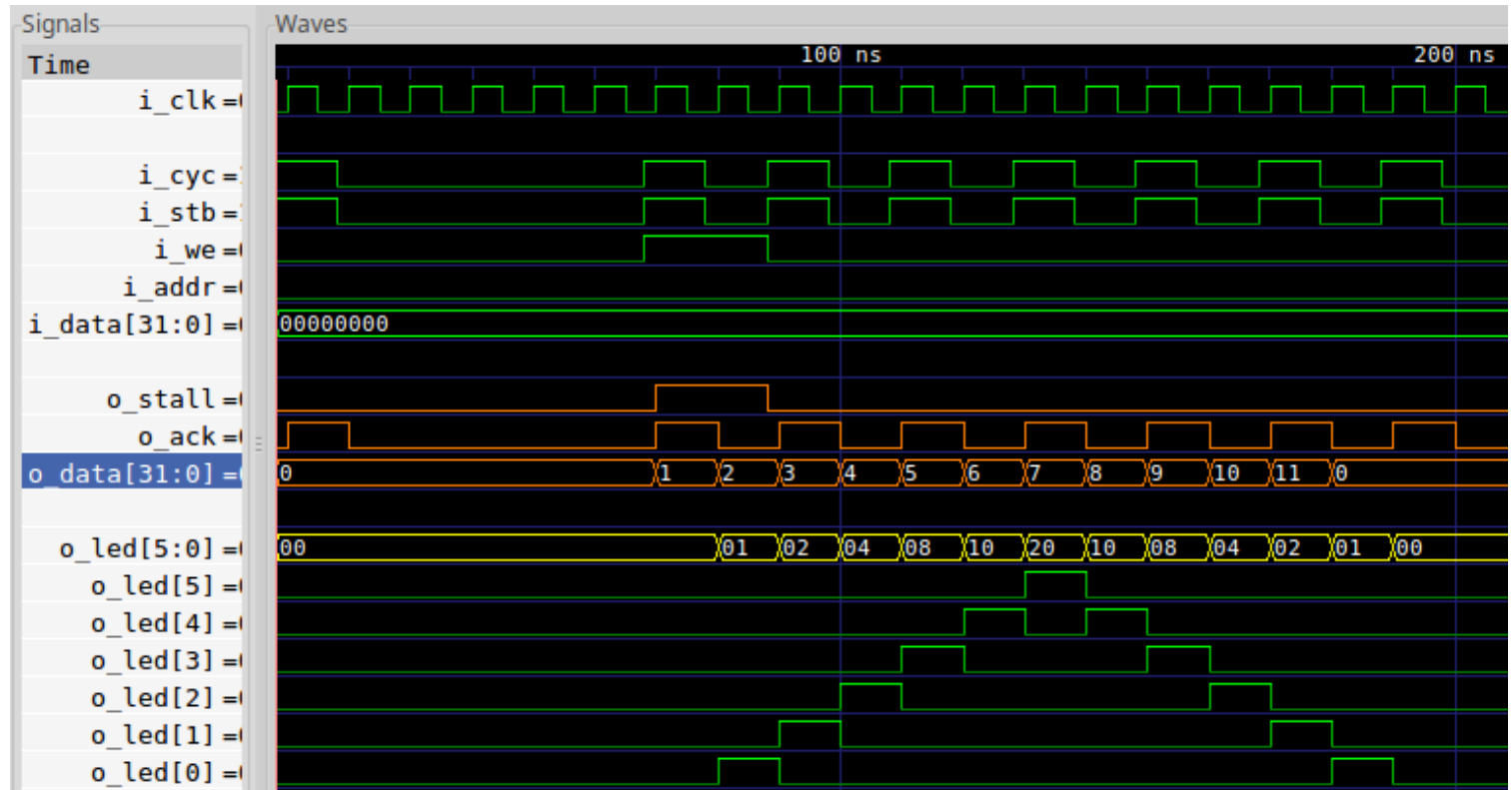


- Pattern: i_stb, o_ack repeats
- Lesson: The clock ticks twice per read



Sim Exercise



Here's the full and final simulation

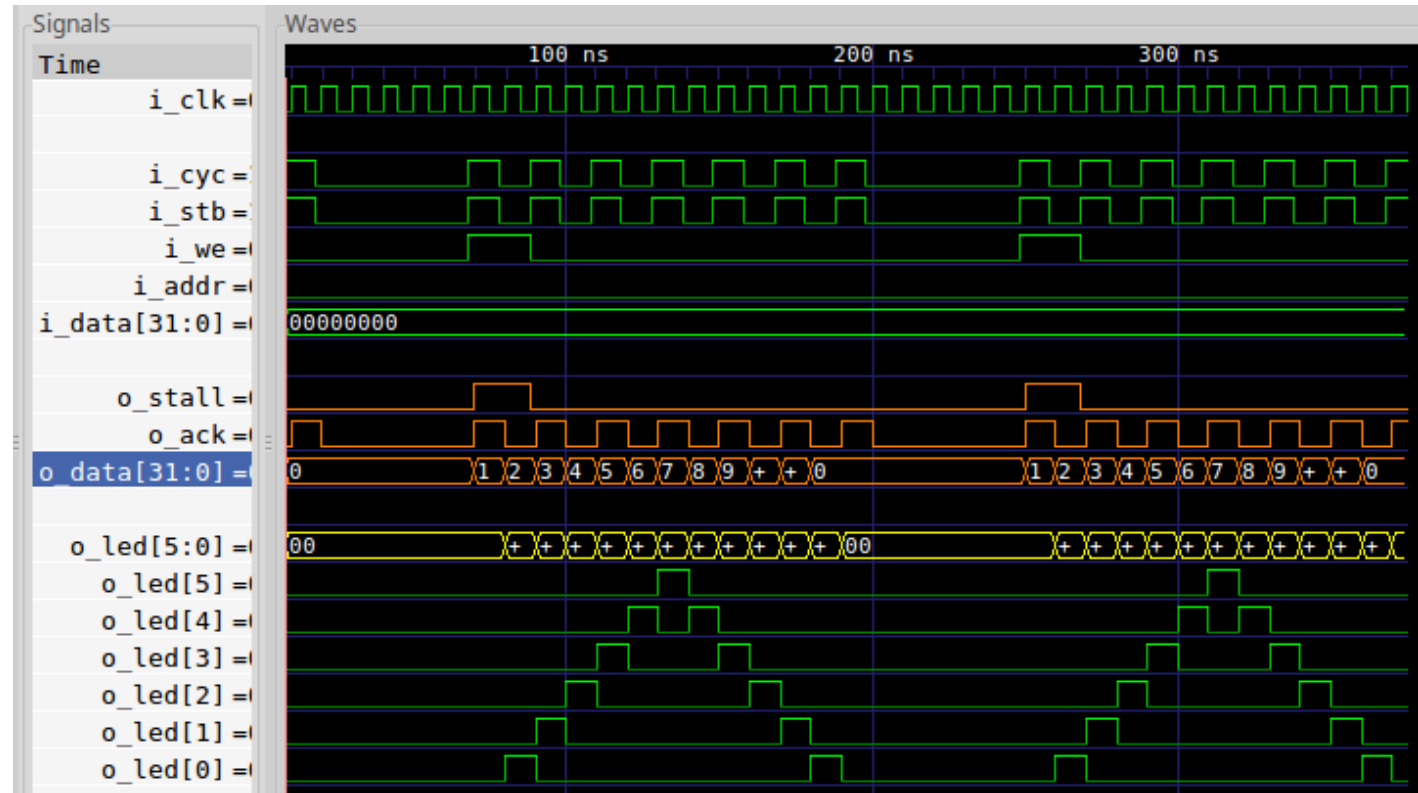

Here you can see both LED walks, as expected



Formal past operator



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

▷ Past Operator

Formal Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

Pipeline logic needs to reason in passing time

- **\$past**(X) returns the value of X one clock ago
- **\$past**(X,N) returns the value of X *N* clocks ago
- Both require a clock

```
always @(posedge i_clk)
  if ($past(C))
    assert(X == Y);
```

- It's illegal to use **\$past**(X) without a clock

```
// This is an error: there's no clock
always @(*)
  if ($past(C))
    assert(X);
```



Formal past operator



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- ▷ Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

\$past(X) has one disadvantage

- On the initial clock, **\$past**(X) is undefined
 - Assertions referencing **\$past**(X) will always fail
 - Assumptions referencing **\$past**(X) will always succeed
- I guard against this with f_past_valid

```
reg      f_past_valid;  
initial f_past_valid = 0;  
always @(posedge i_clk)  
    f_past_valid = 1'b1;
```

- To use, place f_past_valid in an **if** condition

```
always @(posedge i_clk)  
if ((f_past_valid)&&($past(some_condition)))  
    assert(this_must_then_be_true);
```



Formal Verification



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
 - Formal
 - ▷ Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

What properties might we use?

- **assume** properties of the inputs
- **assert** properties of local states and outputs




Formal Verification



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal
 - ▷ Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

What properties might we use?

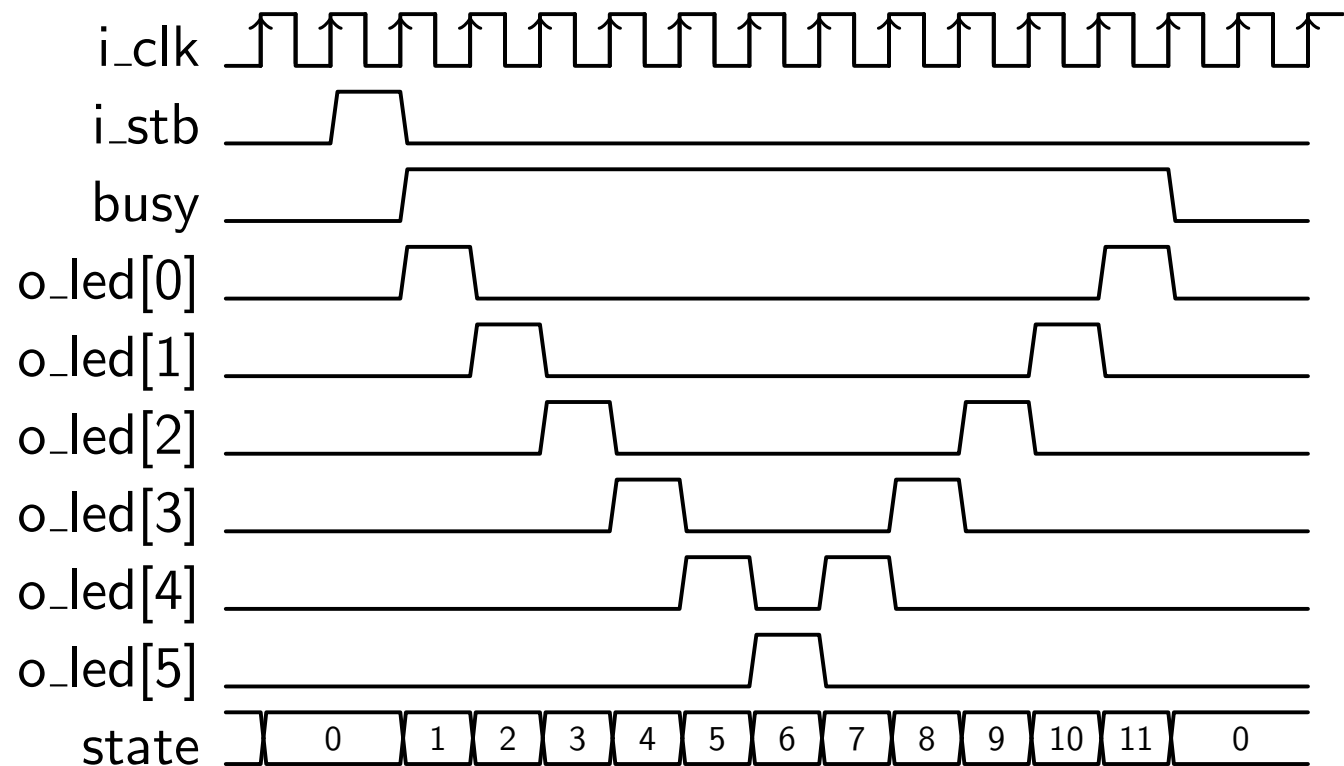

The goal waveform diagram should give you an idea



Formal Verification



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

What properties might we use?

- For our state machine

```
always @(*)
case(state)
4'h0: assert(o_led == 0);
4'h1: assert(o_led == 6'h1);
4'h2: assert(o_led == 6'h2);
//
4'hb: assert(o_led == 6'h1);
endcase

always @(*)
    assert(busy != (state == 0));

always @(*)
    assert(state <= 4'hb);
```




Formal Verification



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

What properties might we use?

- For our state machine, using **\$past**(X)
- An accepted write should start our cycle

```
always @(posedge i_clk)
if ((f_past_valid)&&(b$past(i_stb))
      &&(b$past(i_we))&&(b!$past(o_stall)))
begin
    assert(state == 1);
    assert(busy);
end
```



Formal Verification



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

What properties might we use?

- During the cycle, the state should increment

```
always @(posedge i_clk)
if ((f_past_valid)&&($past(busy))
      &&($past(state < 4'hb)))
    assert(state == $past(state)+1);
```



Formal Verification



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

What properties might we use?

- For our bus interface?

```
// Bus should be idle initially
```

```
initial assume (!i_cyc);
```

```
// i_stb is only allowed if i_cyc
```

```
always @(*)
```

```
if (!i_cyc)
```

```
    assume (!i_stb);
```

```
// When i_cyc goes high, so too does i_stb
```

```
always @(posedge i_clk)
```

```
if ((!$past(i_cyc))&&(i_cyc))
```

```
    assume (i_stb);
```



Formal Verification



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

What properties might we use?

- For our bus interface?

```
always @(posedge i_clk)
  if ((f_past_valid)&&($past(i_stb))
      &&($past(busy)))
  begin
    // Request is stalled
    // It shouldn't change
    assume(i_stb);
    assume(i_we == $past(i_we));
    assume(i_addr == $past(i_addr));
    if (i_we)
      assume(i_data == $past(i_data));
  end
```



Formal Verification



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
 - Formal
 - ▷ Verification
- SymbiYosys Tasks
- Exercise
- Bonus
- Conclusion

What properties might we use?

- For our bus interface?

```
always @(posedge i_clk)
if ((f_past_valid)&&($past(i_stb))
      &&(!$past(o_stall)))
    assert(o_ack);
```



Cover Property



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal

▷ Verification

SymbiYosys Tasks

Exercise

Bonus

Conclusion

You can also use **\$past** with **cover**

```
always @(posedge i_clk)
if (f_past_valid)
    cover ((!busy)&&($past(busy)));
```



SymbiYosys Tasks



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
 - SymbiYosys
 - ▷ Tasks
- Exercise
- Bonus
- Conclusion

Constantly editing our SymbiYosys file is getting old

- Running cover, then
- Editing our script, then
- Running induction, then ...
- Can we do this with one file?

Yes, using SymbiYosys tasks!

- SymbiYosys allows us to define multiple different scripts
- ... all in the same file
- It does this using tasks



SymbiYosys Tasks



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
 - SymbiYosys
 - ▷ Tasks
- Exercise
- Bonus
- Conclusion

Let's define two tasks

- `cvr` to run cover
- `prf` to run induction

SymbiYosys lines prefixed by a task name are specific to that task

```
[ tasks ]
prf
cvr

[ options ]
cvr: mode cover
prf: mode prove
```

The full `reqwalker.sby` file is with the course handouts



SymbiYosys Tasks



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
 - SymbiYosys
 - ▷ Tasks
- Exercise
- Bonus
- Conclusion

We can now run a named task

```
% sby -f reqwalker.sby prf
```

...or all tasks in sequence

```
% sby -f reqwalker.sby
```



SymbiYosys Tasks



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
 - SymbiYosys
 - ▷ Tasks
- Exercise
- Bonus
- Conclusion

I use this often with the ZipCPU

- Using the yosys command hierarchy I can describe multiple configurations to verify
 - With/Without the pipeline
 - With/Without the instruction cache
 - With/Without the data cache
 - ... , etc.
- SymbiYosys tasks are very useful!



Exercise



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
 - ▷ Exercise
- Bonus
- Conclusion

Your turn! Formally verify this design

- Build and create a SymbiYosys script
- Apply to the example design
- Adjust the design until it passes
 - Did you find any bugs?
 - Why weren't these bugs caught in simulation?



Exercise



Lesson Overview

LED Walker

Diagrams

Pipeline

Bus

Wishbone Bus

Simulation

Unused Logic

Sim Exercise

Past Operator

Formal Verification

SymbiYosys Tasks

▷ Exercise

Bonus

Conclusion

Your turn to design

- *Add the integer clock divider to this design*

(Otherwise you'd never see the LED's change on real hardware)

- Adjust both simulator and formal properties
 - Create a simulation trace
 - Create a cover trace
- Do they match?*



Bonus



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
 - ▷ Bonus
- Conclusion

Bonus: If you have hardware with more than one LED ...

- Adjust the number of LED's to match your hardware
- Create an `i_btn` input and connect it to a button
- Replace the `i_stb` input with the logic below

```
reg      stb;
initial  stb = 0;
always  @(posedge i_clk)
if (i_btn)
    stb <= 1'b1;
else if (!busy)
    stb <= 1'b0;
```



Bonus



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
 - ▷ Bonus
- Conclusion

Bonus: If you have hardware with more than one LED

- Adjust the number of LED's to match your hardware
- Create an `i_btn` input and connect it to a button
- Replace the `i_stb` input with the given logic
- Tie `i_we` high
- Ignore `o_stall`, `i_cyc`, etc.

You'll need to adjust the formal properties

You should still be able to simulate it

- Simulate this updated design
- Implement it on your hardware
 - Did it do what you expected? Why or why not?
 - Does the LED walk back and forth when you press the button?
It should!
It **might not work reliably** ... yet



Conclusion



- Lesson Overview
- LED Walker
- Diagrams
- Pipeline
- Bus
- Wishbone Bus
- Simulation
- Unused Logic
- Sim Exercise
- Past Operator
- Formal Verification
- SymbiYosys Tasks
- Exercise
- Bonus
 - ▷ Conclusion

What did we learn this lesson?

- Pipeline handshaking, `i_request` && `!o_busy`
- State transition diagrams
- Definition of a bus
- Logic involved in processing the wishbone bus
- How to make a wishbone slave
- How to make wishbone bus calls from your Verilator C++ driver
- How to ignore unused logic in Verilator
- Verilator requires a call to `eval()` for combinatorial logic to settle
- The **\$past** operator in formal verification
- SymbiYosys tasks